

Bioelectricity

Coulombs Law

Coulombs electric force $F_e = k_e \frac{|q_1||q_2|}{r^2}$

Charge
distance
Coulombs Constant
 $k_e = \frac{1}{4\pi\epsilon_0}$

$$k_e = 9 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$$

- **Current** $\Rightarrow$ the rate at which the charge flows through a surface

$I = \frac{Q}{t}$

Current
A $\rightarrow$ ampere
Charge
C $\rightarrow$ Coulomb
time

$V = \frac{I}{n \cdot e \cdot A}$

drift velocity
Current
Cross sectional area
charge of neutron & electron

$J = \frac{I}{A}$

Current density
Current
C.S. Area

• Resistance & Ohm's Law

$$V = IR$$

voltage difference $\rightarrow$ volt
 Current $\rightarrow$ Resistance $\rightarrow \Omega \rightarrow$ ohm

$\rightarrow$ When talked about with temperature:

$$R_T = R_0 (1 + \alpha (T - T_0))$$

where α is the temperature coefficient of resistance

$$P_T = P_0 (1 + \alpha (T - T_0))$$

$$R = \rho \frac{L}{A}$$

Resistance $\rightarrow$ ρ resistivity (changes for diff. substances) (given)
 L length of wire
 A C.S. Area

• Electric Power

- Power $\Rightarrow$ work done per unit time

$$P = I \Delta V$$

$\Delta V = IR$

$\rightarrow$ used to find Power in a load Resistor

$$P = I^2 r$$

$\rightarrow$ used to find power in internal Resistor

$$P = \frac{V^2}{R}$$

$\rightarrow$ used to find Load Resistor

• Electromotive force (emf) (battery)

$$\mathcal{E} = V_R + V_r$$

load $\rightarrow V_R = IR$
 internal $\rightarrow V_r = Ir$

$$\therefore I = \frac{\mathcal{E}}{R + r}$$

$$V = \mathcal{E} - Ir$$

Terminal voltage

$$\Delta V = \mathcal{E} - Ir$$

Potential difference

Simple Resistive Circuits

Series

$$R_{eq} = R_1 + R_2 + R_3$$

Parallel

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

• Same Potential difference (ΔV)

The Capacitor → combination of two conductors

Capacitance of Capacitor $C = \frac{Q}{\Delta V}$

Q → Charge
 ΔV → potential difference

F → Farad

↳ called plates

Parallel Plate Capacitor

Capacitance $C = \frac{k \epsilon_0 A}{d}$

k → dielectric constant (sometimes absent)
 ϵ_0 → Epsilon
 A → Surface Area
 d → distance

- Epsilon → the permittivity of the medium

RC Circuits

↳ Current is not constant

↳ series of resistors & capacitors

Charging a Capacitor

↳ $t < 0$ capacitor doesn't push back against current

Current is located at resistor

↳ the voltages across the resistor and the capacitor will change with time

$$I(t) = \frac{\mathcal{E}}{R} e^{-t/RC}$$

$$V_C(t) = \mathcal{E}(1 - e^{-t/RC})$$

$$Q = 0 \text{ @ } t = 0$$

$$I_{max} = \mathcal{E}/R \text{ @ } t = 0$$

$$\max Q \text{ @ } t \rightarrow \infty$$

$$I_{min} = 0 \text{ @ } t \rightarrow \infty$$

$$Q = C\mathcal{E}$$

$$\tau = RC$$

↳ time constant

$$Q = C\mathcal{E}$$

↳ max charge

$$I_0 = \frac{\mathcal{E}}{R}$$

max charging current

$$q(t) = Q(1 - e^{-t/RC})$$

$$I(t) = I_0 e^{-t/RC}$$

↳ Charge and current
as a function of time

Discharging a Capacitor

↳ $t=0$ Capacitor begins to discharge through the resistor

$$\frac{q(t)}{C} + I(t)R = 0$$

$$\Rightarrow |q(t)| = Q e^{-t/RC}$$

$$\Rightarrow |I(t)| = -I_0 e^{-t/RC}$$

$$I_0 = Q/RC$$

• negative sign = discharging current
direction is opposite of
the one charging

$$V_C(t) = V_0 e^{-t/RC}$$

$$\text{@ } t=RC \rightarrow V_C(t) = \frac{V_0}{e}$$

• Nerve Conduction

Nernst equation → Potential difference across the membrane

$$V = \pm 2.3 \frac{k_B T}{q} \log \left(\frac{C_o}{C_i} \right)$$

Thermal energy

concentration of ions inside & outside

$$\rightarrow \pm 2.3 \frac{1.38 \times 10^{-23} \cdot 310 \text{ K}}{1.6 \times 10^{-19} \text{ C}} \log \left(\frac{C_o}{C_i} \right)$$

electronic charge

$$V = \pm 61.4 \times 10^{-3} \log \left(\frac{C_o}{C_i} \right)$$

• Resistance

$$R_a = \rho \frac{L}{\pi r^2}$$

← of axoplasm

Cross-sectional area

$$R_m = \frac{\rho_m}{2\pi r l}$$

← of membran

Surface area

Space parameter $\lambda \Rightarrow$ how impulse signals travel along the axon before the leakage is complete

$$\rightarrow R_m = R$$

$$\Rightarrow \lambda = \sqrt{\frac{R_m}{R}}$$

$$\lambda = \sqrt{\frac{\rho_m r}{2\rho_a}}$$

usually 0.05-0.7 cm

• Capacitance

$$C = \frac{\epsilon A}{d}$$

$\leftarrow k\epsilon_0$

C for unmyelinated axon
= 10^{-2} F/m^2

C for myelinated axon
= $5 \times 10^{-5} \text{ F/m}^2$

Unmyelinated

Myelinated

R	R_a	$2 \Omega \cdot m$	$2 \Omega \cdot m$
axial resistivity	ρ_{UA}	$0.2 \Omega \cdot m^2$	$40 \Omega \cdot m^2$
axial $\frac{C}{A}$	$\frac{C}{A}$	$10^{-2} F/m^2$	$5 \times 10^{-6} F/m^2$

Propagation speed

$$V(t) = V_0 (1 - e^{-t/R_a C})$$

↳ resting potential

Charging time $\tau = R_a C$

$$v = \frac{1}{2 C_m R_a} \rightarrow \text{length of each unit}$$

membrane capacitance C_m resistivity R_a

↳ the wider the axon, the faster the axonal speed of propagation